


①

Convolutional Codes

memory cells Electronic circuit capable of holding 1-bit information

Memory cells are nothing but flip-flops.

Ex^o D-flip flop

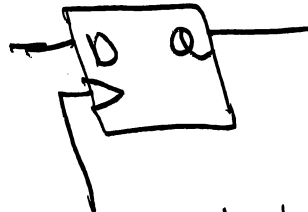

CP → clock pulse


When CP

$$Q(t+1) = D$$


D	Q(t+1)
0	0
1	1

$$\rightarrow Q(t+1) = D$$

↓
output of flip-flop after clock pulse.

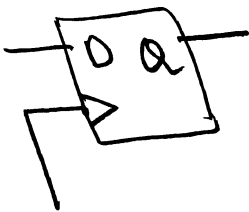


≡

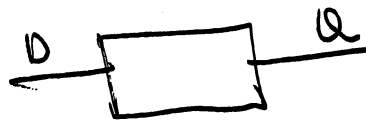

↓ memory cell graphical illustration.

A convolutional encoder consists of memory cells and mod-2 summers.

Ex^o

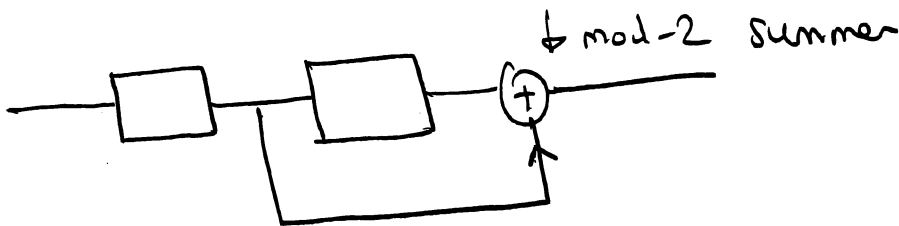

In memory cells Clock-pulse is not shown we trace the memory cells behaviour by giving ~~input~~ virtual clocks by ourselves

(2)

Ex:




$a = 10110$ find memory cell output at each clock

Sln:

$a = 10110$

↓ first bit to be sent to the cell

Initially

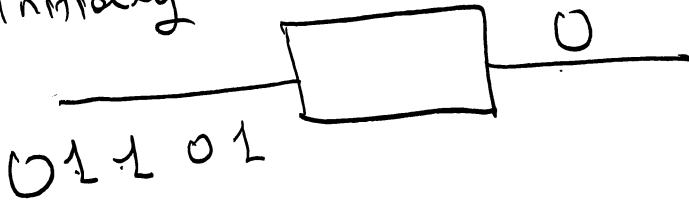


CP1:




CP2:




CP3:

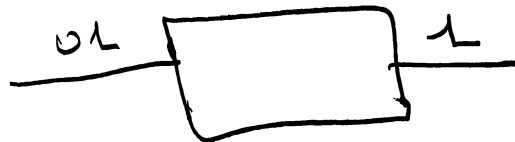

CP4:

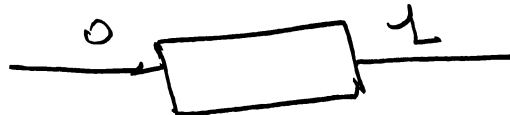

CP5

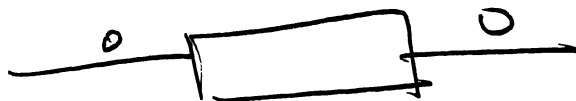


In general $b_1 b_2$ c

after clock pulse



3

Exo

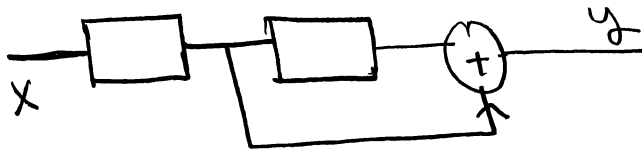


$X = 1011$

find Y


Solⁿ

Initially


Initial outputs of the cells are zero

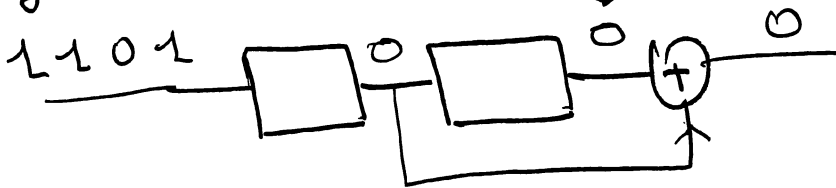


After CP1:

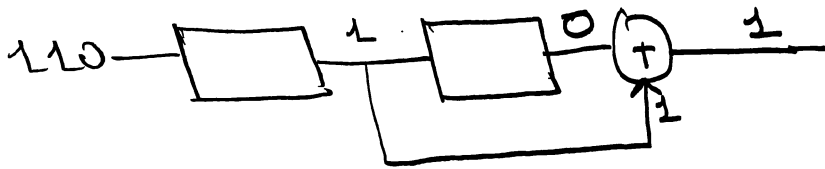


After CP2:

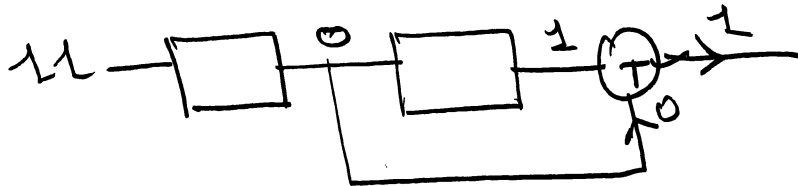

After CP3:

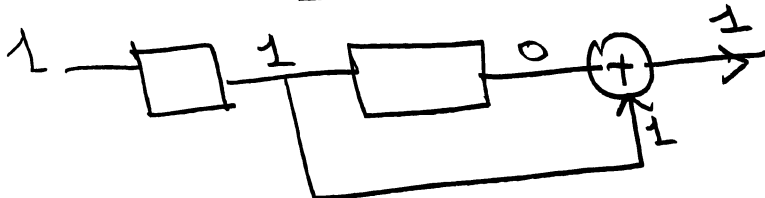


After CP4:

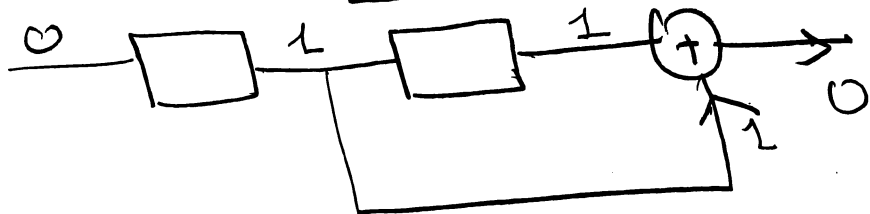

Hence output string is

1110

Remarks

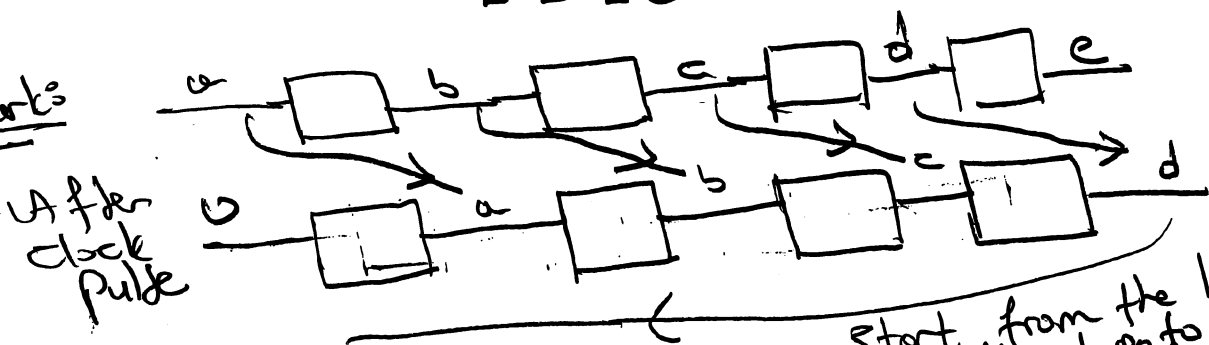


After clock pulse

start from the last cell and go to the first one.

④ Impulse response of a convolutional encoder

If your input is $1000\dots 0$ your output is called impulse response

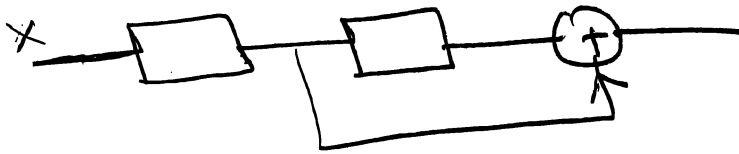Ex^o Find the impulse response of the following convolutional encoder



Sln^o

Input is $x = 10$

only 2-bits


Since convolutional encoder includes 2-memory cells

In general


$x = 10\dots 0$
m-bits

m is the number of memory cells


Initially

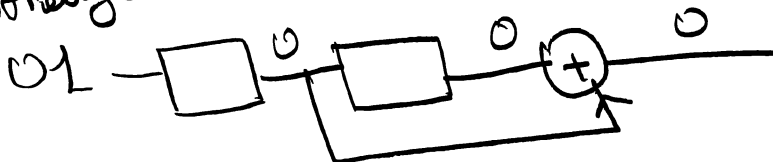

After $t=1$

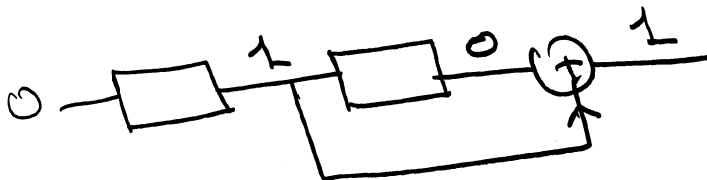


After $t=2$

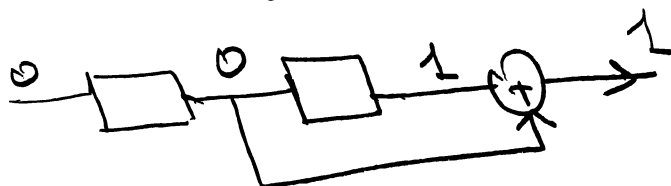

Output is 011

Hence, impulse response is 011

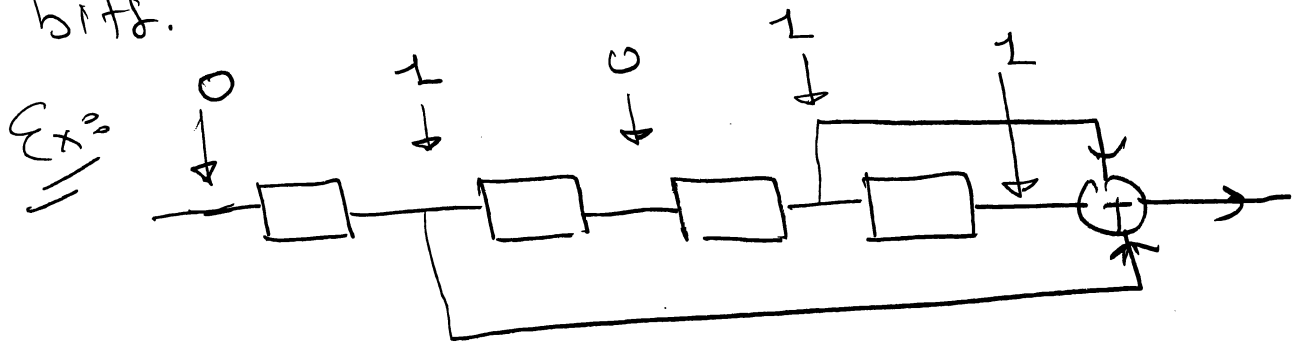5) Easy way of finding the impulse response
 Check the connection between output of a cell
 and final output if there is a connection
 write 1 otherwise write 0, and collect the
 bits.



Impulse response is 01011

Convolution:

$$x = 1011$$

$$y = 110$$

Find $x \otimes y$ → convolution
 of x & y

Take one of them and write it

e.g. 1011 → x is taken

reverse the other

011 → y is reversed.

Compute the convolution as follows

$$\begin{array}{l} 1011 \\ 011 \end{array} \left. \vphantom{\begin{array}{l} 1011 \\ 011 \end{array}} \right\} \rightarrow \text{product, and mod-2 sum} \\ \text{gives 1}$$

$$\begin{array}{l} 1011 \\ 011 \end{array} \left. \vphantom{\begin{array}{l} 1011 \\ 011 \end{array}} \right\} \rightarrow 1$$

$$\begin{array}{l} 1011 \\ 011 \end{array} \left. \vphantom{\begin{array}{l} 1011 \\ 011 \end{array}} \right\} \rightarrow 1$$

6

$$\left. \begin{array}{l} 1011 \\ 011 \end{array} \right\} \rightarrow 1+1 \Rightarrow 0$$

$$\left. \begin{array}{l} 1011 \\ 011 \end{array} \right\} \rightarrow 1$$

$$\left. \begin{array}{l} 1011 \\ 011 \end{array} \right\} \rightarrow 0$$


So output is 111010

Remarks If you know the impulse response of a convolutional code, for an arbitrary string x the output of the convolutional encoder can be found as

$$y = x * h$$

↓ impulse response

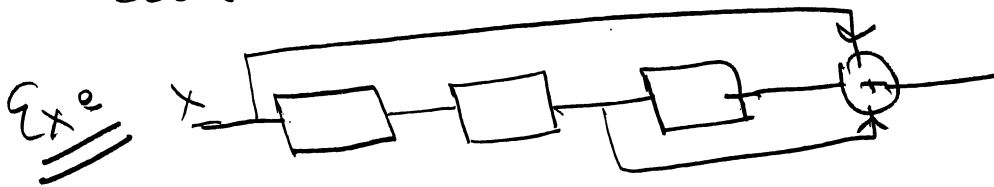This is why they are called as convolutional codes.




If $x = 111011$ find output of the encoder
↓
first bit

Slns

We can compute the output bit every clock pulse and collect the output bits and find the output string

⑦

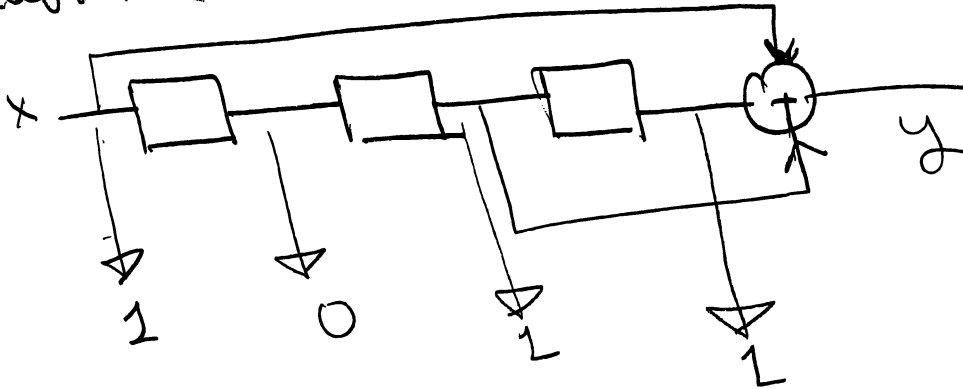or lets first the impulse response of the convolutional encoder



$h = (1011) \rightarrow$ impulse response.


$x = (11011) \rightarrow$ input

$y = x \otimes h \rightarrow$

1101	}	→ 0
		11011

go on like this

Recursive Convolutional Encoders

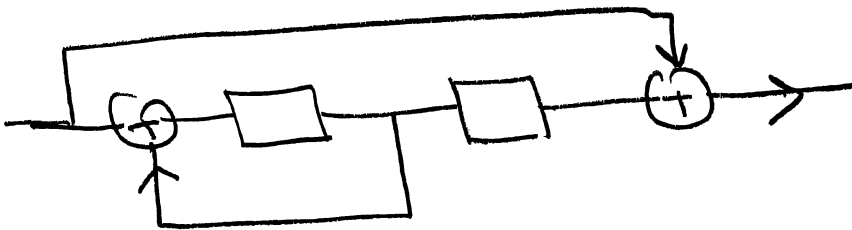


↓ If a convolutional encoder includes a feedback it is a recursive convolutional encoder.

Recursive convolutional encoders may have infinite impulse response
 i.e., $h = 10110\dots\dots$

8) A convolutional encoder may have more than one input stream and more than one output stream

Ex 3

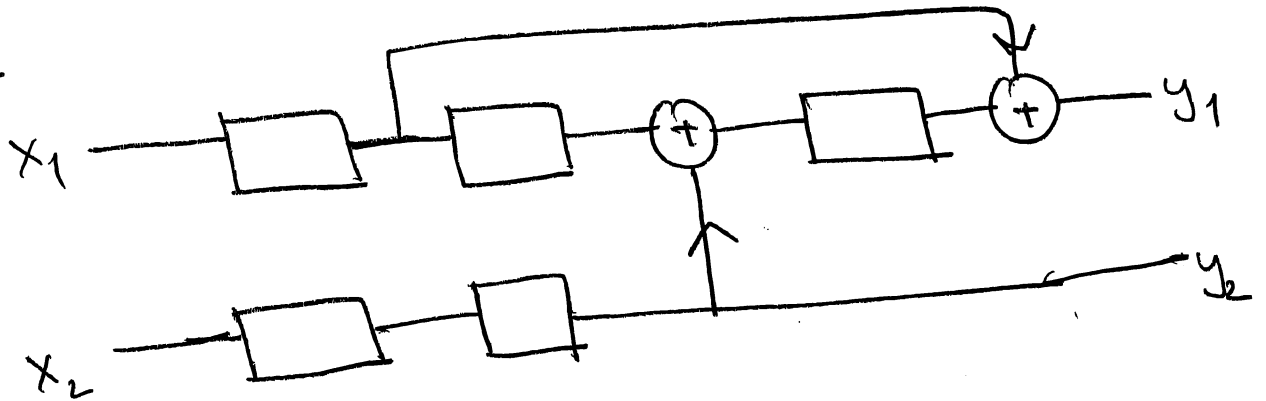

In this case an impulse response is defined between every input and every output pair

i.e.,

Impulse responses between

$$X_1 - Y_1 \rightarrow h_1$$

$$X_1 - Y_2 \rightarrow h_2$$

$$X_2 - Y_1 \rightarrow h_3$$

$$X_2 - Y_2 \rightarrow h_4$$

4-impulse responses

$$h_1 = 0101 \rightarrow X_1 = 1000 \rightarrow \text{output } Y_1 = 0101$$

$$h_2 = 0000 \rightarrow X_1 = 1000 \rightarrow \text{output } Y_2 = 0000$$


$$h_3 = 0010 \rightarrow X_2 = 10 \rightarrow \text{output } Y_1 = 0010$$

$$h_4 = 0010 \rightarrow X_2 = 10 \rightarrow \text{output } Y_2 = 0010$$

9A

Ex:

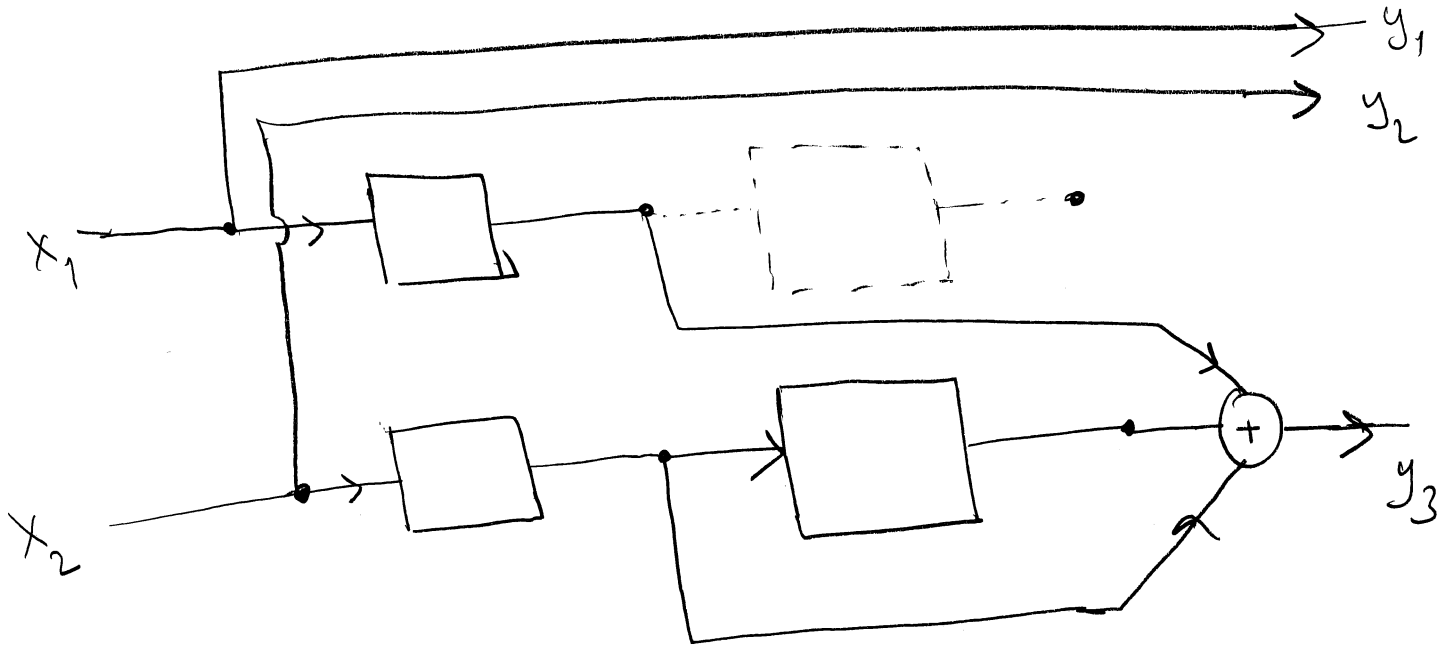Find all impulse responses for the below encoder



Between $x_1 - y_1$

$$h^{11} = 100 \rightarrow h^{11} = (4)_{\text{octal}}$$

$$x_1 - y_2 \quad h^{12} = 000 \rightarrow h^{12} = (0)_{\text{octal}}$$

$$x_1 - y_3 \quad h^{13} = 010 \rightarrow h^{13} = (2)_{\text{octal}}$$

$$x_2 - y_1 \quad h^{21} = 000 \rightarrow h^{21} = (0)_{\text{octal}}$$

$$x_2 - y_2 \quad h^{22} = 100 \rightarrow h^{22} = (4)_{\text{octal}}$$

$$x_2 - y_3 \quad h^{23} = 011 \rightarrow h^{23} = (3)_{\text{octal}}$$


9B

HW Due To Next Week

HW

Given the convolutional encoder

① below

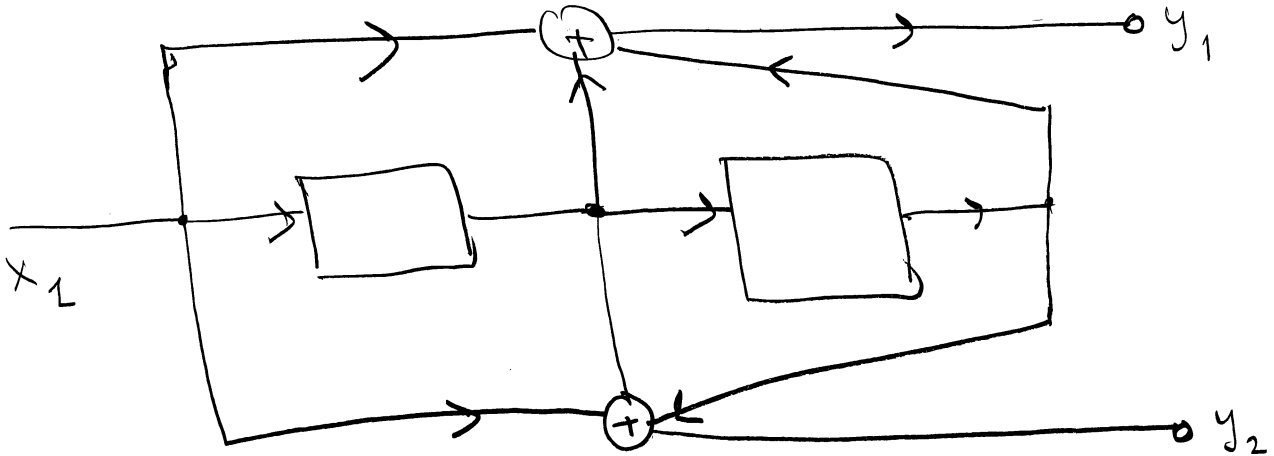


a) Find all the impulse responses between $x_1 - y_1$

$x_1 - y_2$


b) Find y_1 & y_2 for $x_1 = (111101)$

②

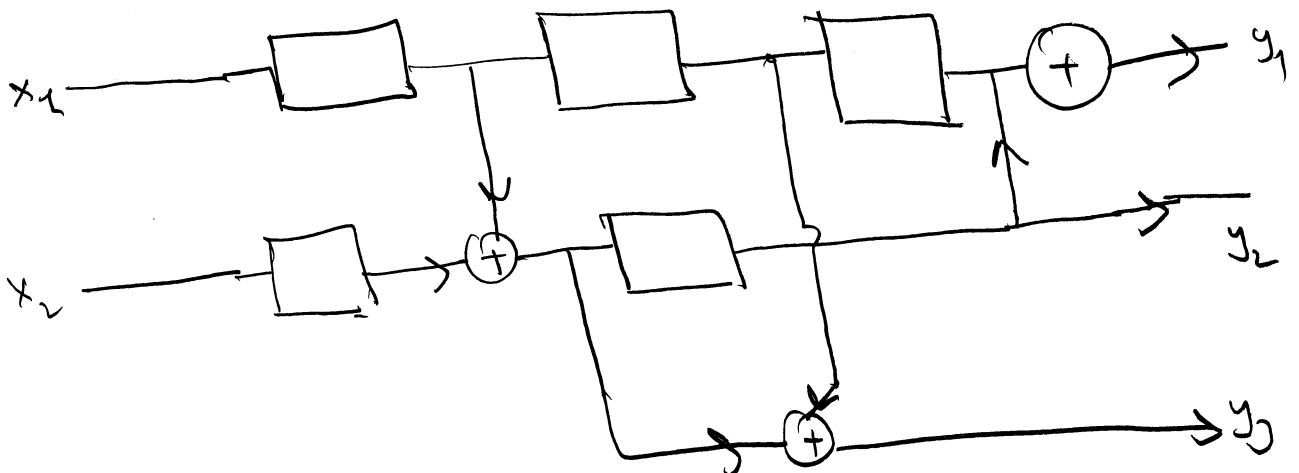

Find all the impulse responses

8

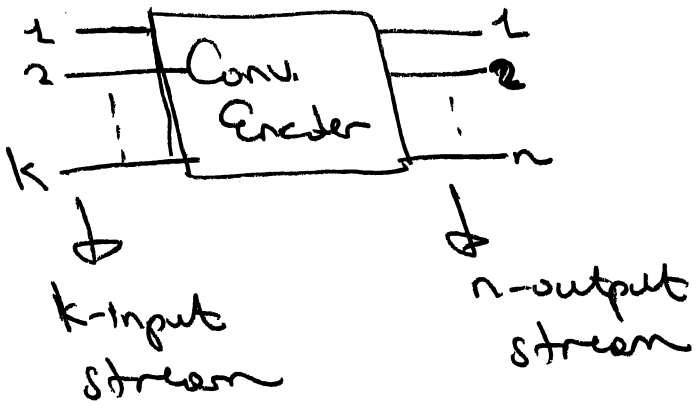

h^{ij} → impulse response between input i and output j

$i = 1 \dots k$

$j = 1 \dots n$

In total there are $k \times n$ impulse responses

Remark If there are m memory cells in a convolutional encoder, the impulse response h^{ij} contains m -bits

h_k^{ij} → k th bit of h^{ij}

Generator matrices for convolutional codes

$c = d \otimes h$ → codeword = dataword \otimes imp. resp.

$c = dG$ → G is constructed from the components of the impulse sequences

10

For an (n, k, m) convolutional code

$k \rightarrow$ number of input ports

$n \rightarrow$ number of output ports

$m \rightarrow$ number of memory cells

G_i is the $k \times n$ matrix

given by


$$G_i = \begin{bmatrix} h_i^{(1,1)} & h_i^{(1,2)} & \dots & h_i^{(1,n)} \\ h_i^{(2,1)} & h_i^{(2,2)} & \dots & h_i^{(2,n)} \\ \vdots & \vdots & \ddots & \vdots \\ h_i^{(k,1)} & h_i^{(k,2)} & \dots & h_i^{(k,n)} \end{bmatrix}$$

The generator matrix G is constructed as

$$G = \begin{bmatrix} G_0 & G_1 & G_2 & \dots & G_m & 0 & 0 & \dots \\ 0 & G_0 & G_1 & \dots & G_m & 0 & 0 & \dots \\ \vdots & \vdots & \vdots & \ddots & \vdots & \vdots & G_m & \vdots \end{bmatrix}$$

Ex

$(4, 3, 2)$ convolutional code

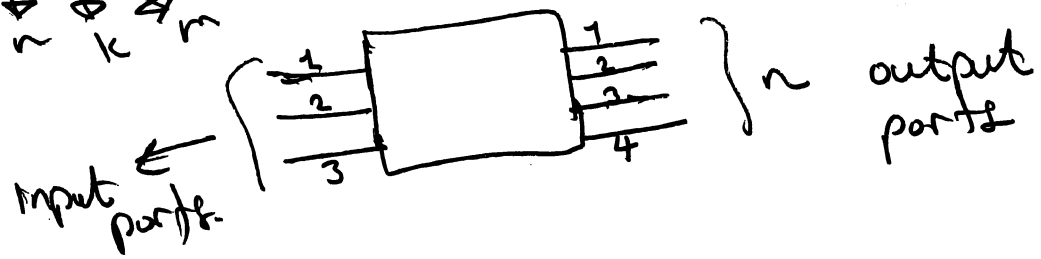

① The impulse responses between input ports and output ports are given as

$$\begin{aligned}
 h^{(1,1)} &= [1 \ 0 \ 0] & h^{(2,1)} &= [0 \ 0 \ 0] & h^{(3,1)} &= [0 \ 0 \ 0] \\
 h^{(1,2)} &= [1 \ 0 \ 0] & h^{(2,2)} &= [1 \ 1 \ 0] & h^{(3,2)} &= [0 \ 1 \ 0] \\
 h^{(1,3)} &= [1 \ 0 \ 0] & h^{(2,3)} &= [0 \ 1 \ 0] & h^{(3,3)} &= [1 \ 0 \ 1] \\
 h^{(1,4)} &= [1 \ 0 \ 0] & h^{(2,4)} &= [1 \ 0 \ 0] & h^{(3,4)} &= [1 \ 0 \ 1]
 \end{aligned}$$

$$G_0 = \begin{bmatrix} 1 & 1 & 1 & 1 \\ 0 & 1 & 0 & 1 \\ 0 & 0 & 1 & 1 \end{bmatrix}$$

$$G_1 = \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & 1 & 1 & 0 \\ 0 & 1 & 0 & 0 \end{bmatrix} \quad G_2 = \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 1 \end{bmatrix}$$

in a similar manner as in G_0 , the matrices G_1 & G_3 are formed.


$$G = \begin{bmatrix} G_0 & G_2 & G_2 & 0 & 0 & \dots \\ 0 & G_0 & G_2 & G_2 & 0 & \dots \\ 0 & 0 & G_0 & G_1 & G_2 & \dots \\ \vdots & \vdots & \vdots & \vdots & \vdots & \ddots \end{bmatrix}$$

Size of G depends on information block length.

12

Ex:

For $d = (110 | 011 | 101)$

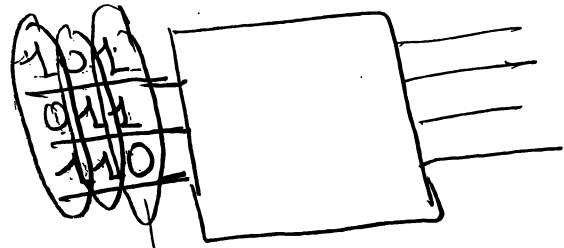

first bit entering into the convolutional encoder

$$G = \begin{bmatrix} G_0 & G_1 & G_2 & \bar{0} & \bar{0} \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \end{bmatrix}$$

where

$$\bar{0} = \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix}$$

$$G_0 = \begin{bmatrix} 1 & 1 & 1 & 1 \\ 0 & 1 & 0 & 1 \\ 0 & 0 & 1 & 1 \end{bmatrix}$$

$$G_1 = \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & 1 & 1 & 0 \\ 0 & 1 & 0 & 0 \end{bmatrix}$$

$$G_2 = \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 1 \end{bmatrix}$$

Generator polynomials for convolutional codes

$$v = u * h \rightarrow v(D) = u(D) \cdot \overbrace{h(D)}$$


polynomial for u

polynomial for h

$h(D)$ is the generator polynomial of the convolutional code and shown by $g(D)$.

13

Ex:

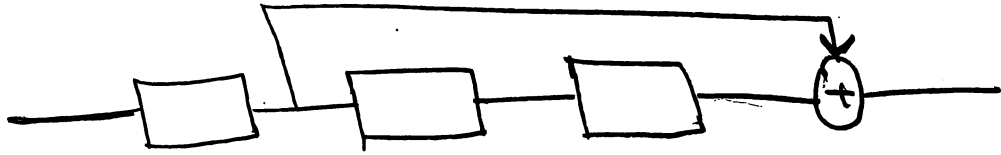


a) $h = ?$ impulse response

b) $h(D) = ?$ (i.e. $g(D) = ?$)

c) encode the bit stream

$d = (1011)$ using $g(D)$

Sl:

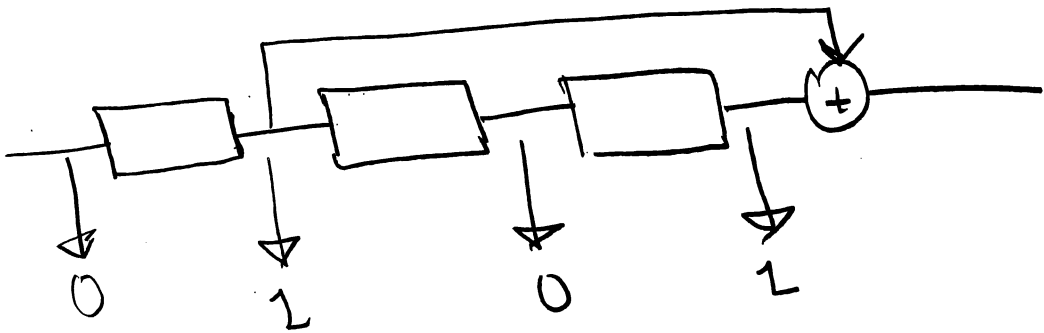

$$h = (0101)$$

$$g(D) = h(D) = D^2 + 1$$

$$d(D) = D^3 + D + 1$$

$$e(D) = g(D) d(D)$$

$$= (D^2 + 1)(D^3 + D + 1)$$

$$= D^5 + \cancel{D^4} + D^2 + \cancel{D} + 1$$

$$= D^5 + D^2 + D + 1$$

$$c = (0100111) \stackrel{?}{\leftarrow} (1011) \oplus (0101)$$

check



14

Remark

$$\text{If } d = (d_0 \ d_1 \ d_2 \ \dots)$$

$$\text{then } d(D) = d_0 + d_1 D + d_2 D^2 + \dots$$

OR if you adopt d as

$$d = (\dots \ d_2 \ d_1 \ d_0)$$

$$d(D) = \dots + d_2 D^2 + d_1 D + d_0$$



adopt one of them for d and h i.e. g

Graphical Representation of Convolutional Codes

States

The contents of the memory cells is accepted as state.
(The content of memory cells = output of memory cells)

Ex:

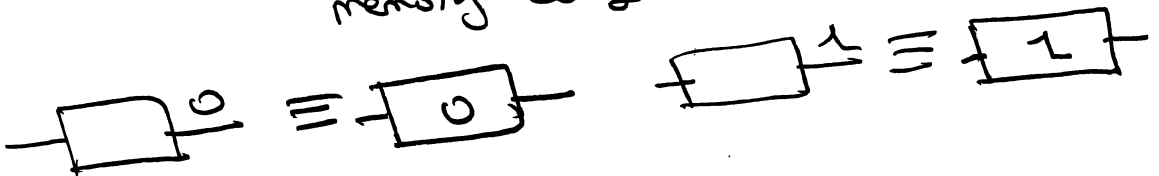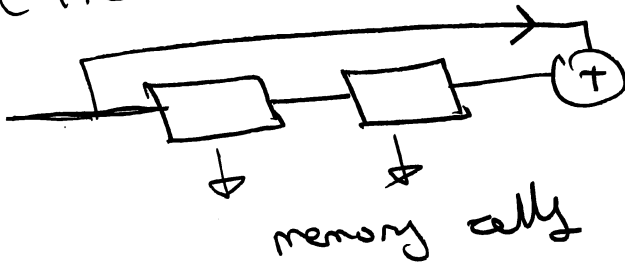


can be

00
01
10
11

states of the conv. encoder.

15


Ex:

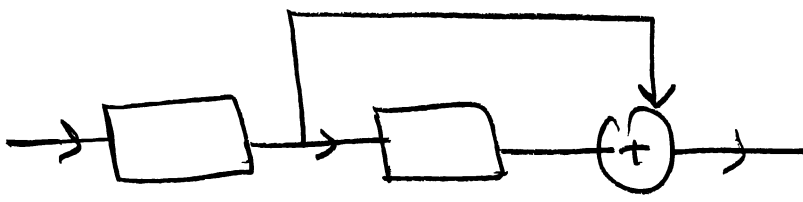

CP → Clock Pulse

Draw state diagram of the above conv. encoder

Slns

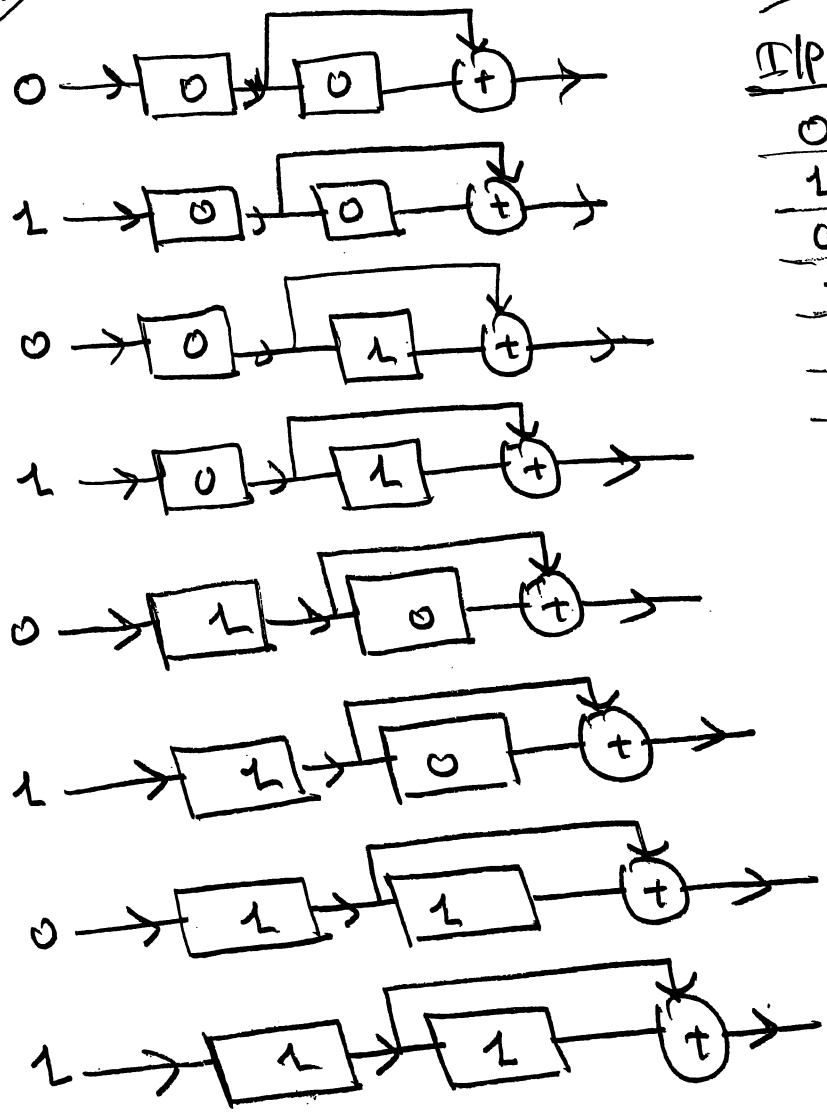


		Before CP	Before CP	After CP
I/P	O/P	Present State	Next State	
0	0	00	00	00
1	0	00	10	10
0	1	01	00	00
1	1	01	10	10
0	1	10	01	01
1	1	10	11	11
0	0	11	01	01
1	0	11	11	11


↓
This table can be expressed using state diagram

16


State diagram of the example is drawn as

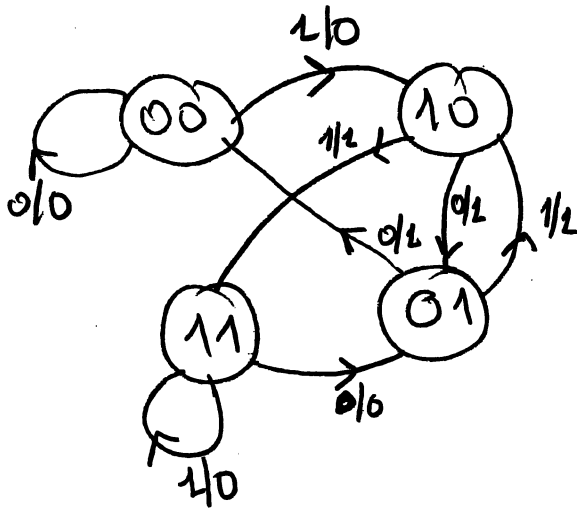

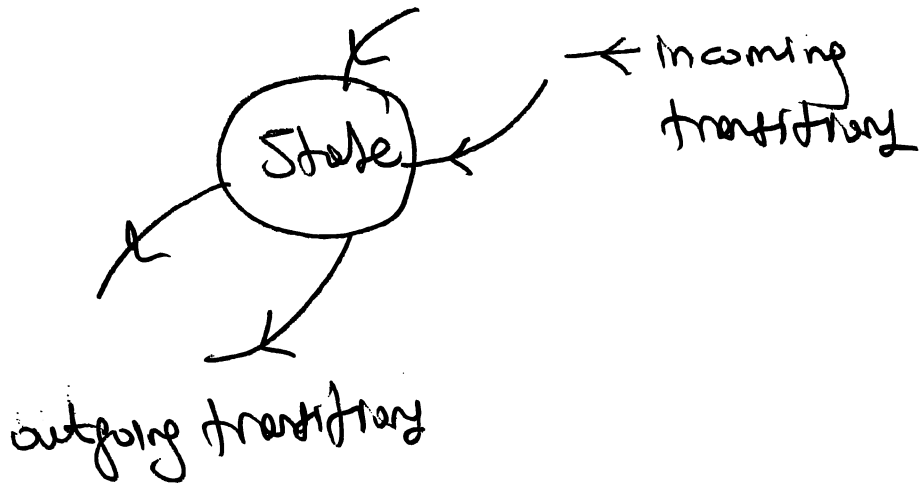Every state has two incoming transitions and two outgoing transitions




17

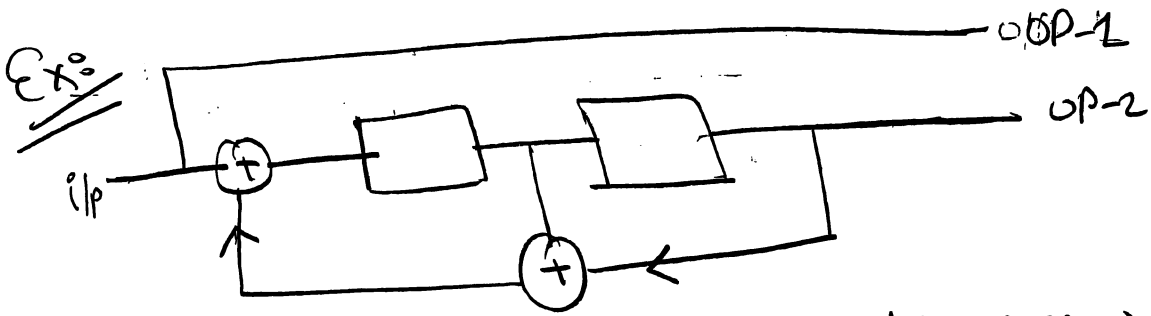


obtain the state transition diagram of the above recursive convolutional encoder

Tree Diagram:

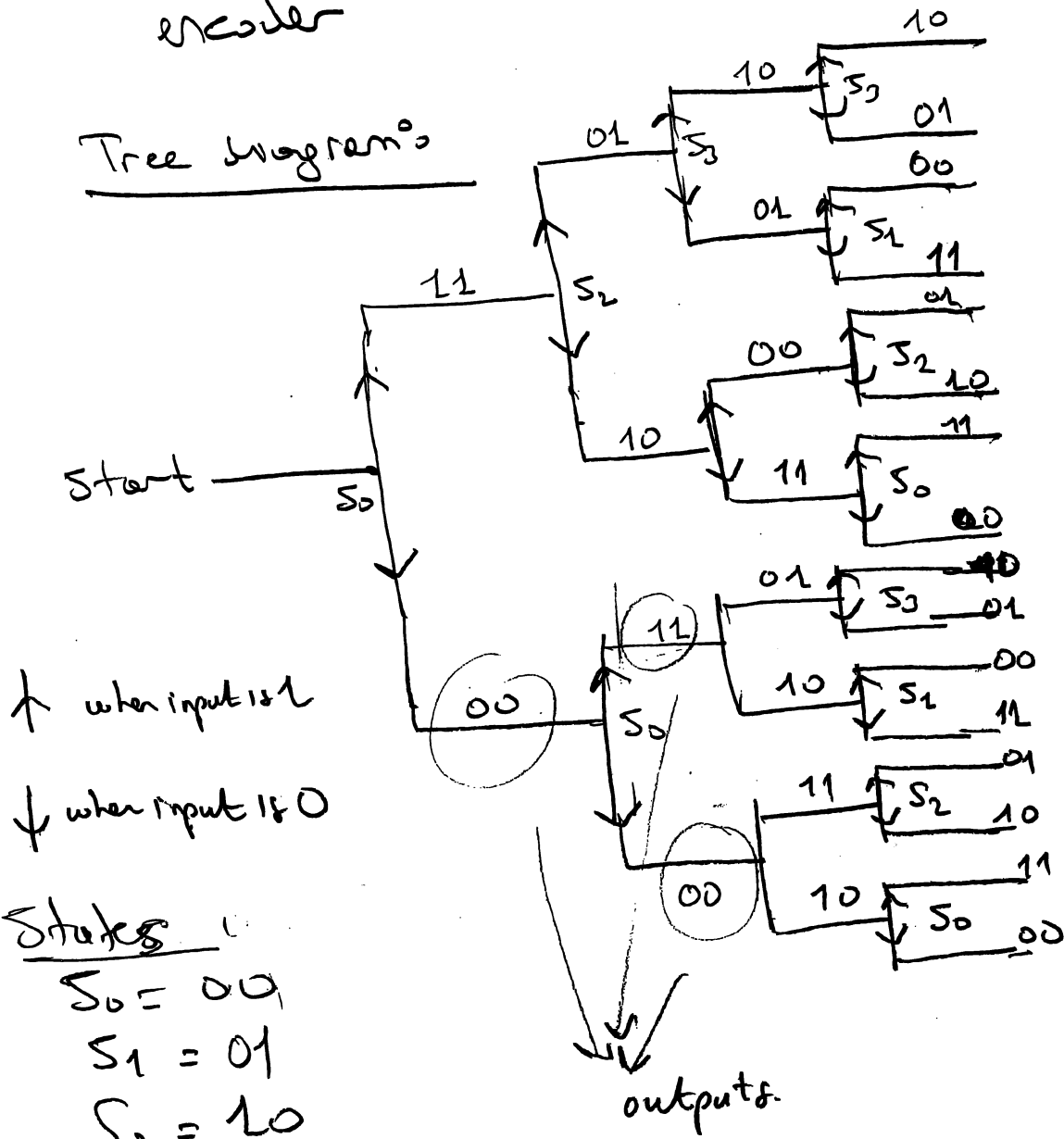

Trellis diagrams

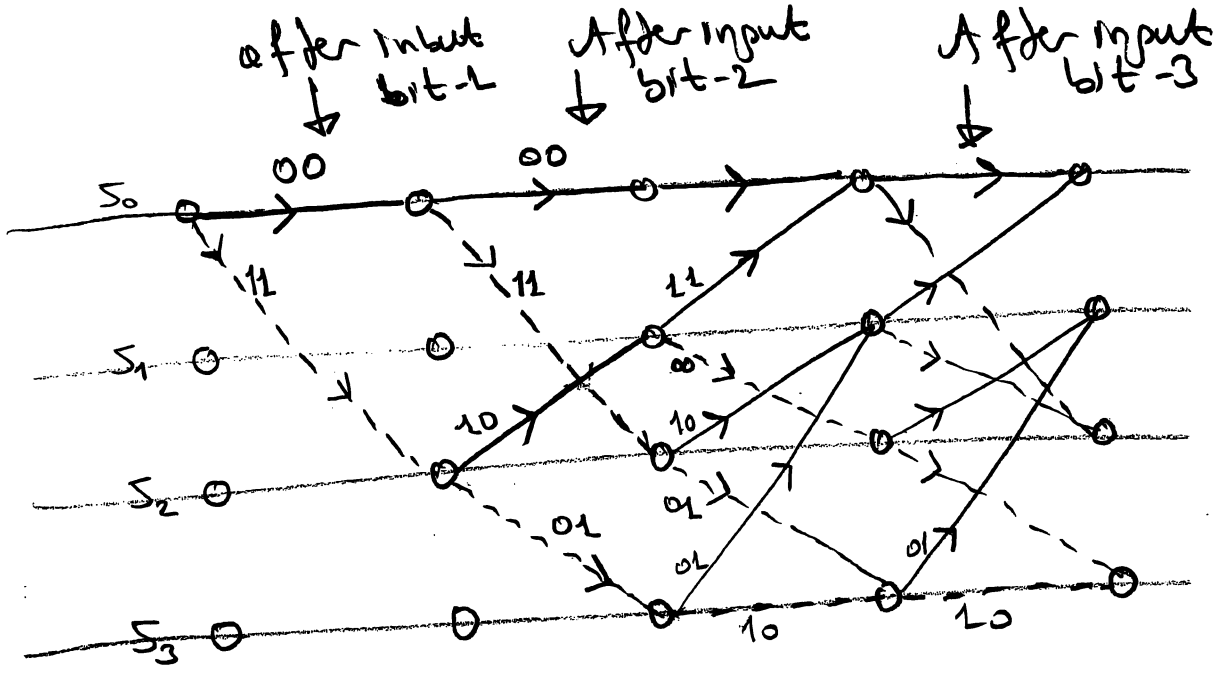
States: $00 \rightarrow S_0$
 $01 \rightarrow S_1$
 $10 \rightarrow S_2$
 $11 \rightarrow S_3$



Initial state is S_0

As a new bit is taken transition to a new state occurs and output bits are formed

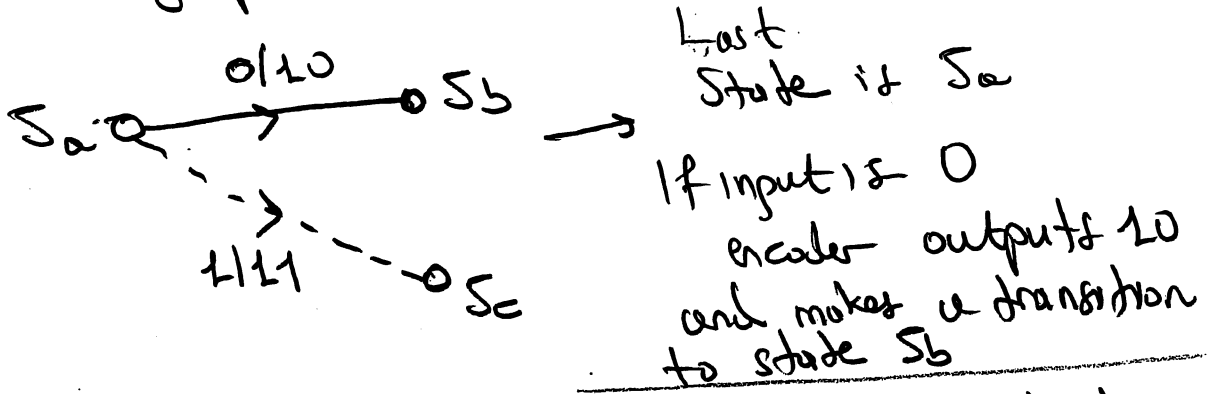In general a state has the following transition graph in trellis diagram



If input is 1, encoder outputs 11 and makes a transition to S_c